



TEACHING
WALLAH

Teaching Exam

Subject – Computer Science

Topic – Digital Logic



Lecture No.- 7

By- Rahul Sir

Topics to be Covered


Topic



 - 1:- Canonical Form – SOP and POS ✓
- 2:- Difference between SOP and POS ✓
- 3:- SOP → K-map (2,3,4 Variable) ✓
- 4:- POS → K-map (2,3,4 Variable) ✓
- 5:- K-Map using Don't CARE ✓



In Boolean algebra, SOP (Sum of Products) and POS (Product of Sums) are two canonical forms used to represent Boolean expressions. SOP is a logical sum (OR) of product terms (AND), while POS is a logical product (AND) of sum terms (OR). These forms are derived from truth tables and provide standardized ways to express Boolean functions.





SOP Vs POS in Digital Logic

Representation of Boolean expression can be primarily done in two ways. They are as follows:

1. Sum of Products (SOP) form
2. Product of Sums (POS) form

$$n=3 \Rightarrow 2^n = 2^3 = 8 \Rightarrow \text{Total Possible of Input}$$

NOTE

If the number of input variables are n , then the total number of combinations in Boolean algebra is 2^n .

$$A = 1 \text{ (High Input)} \\ \bar{A} = 0$$

$$O = \text{Output} = \bar{A}$$

If the input variable (let A) value is :

- Zero (0) - a is LOW -It should be represented as A' (Complement of A)
- One (1) - a is HIGH -It should be represented as A



In Boolean logic,

AND is represented as '.'

A AND B is written as 'A.B'

OR is represented as '+'

A OR B is written as 'A+B'

For example, Considering number of input variables =3, Say A, B and C.

Total number of combinations are: $2^3=8$.



What is SOP?

It is one of the ways of writing a Boolean expression. As the name suggests, it is formed by adding (OR operation) the product terms. These product terms are also called as 'min-terms'. Min-terms are represented with 'm', they are the product(AND operation) of Boolean variables either in normal form or complemented form.



A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

The function X can be written in SOP form by adding all the min-terms when X is HIGH(1).

While writing SOP, the following convention is to be followed:

If variable A is Low(0) - A'
A is High(1) - A

$$Q \Rightarrow \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C$$

$$X(SOP) = \sum m(1, 3, 6) \\ = A'B'C + A'BC + A\bar{B}C$$


SOP Represent Always High

$$\Rightarrow (\bar{A}\bar{B}C) + (\bar{A}BC) + (A\bar{B}C)$$

$\sum$
↓
Sum

$\prod$
↓
Product

$$X(A, B, C) = \sum m(1, 3, 6)$$

 



Find the Expression :-

Q1:- $f(x,y,z) = \Sigma(0,4,6)$

Q2:- $f(x,y,z) = \Sigma(1,5,7)$

Q3:- $f(x,y,z) = \Sigma(1,5)$

$f(A,B,C,D) = \Sigma(1,5,7,8) = \Sigma(m_1, m_5, m_7, m_8)$

$\downarrow$
Sop $\rightarrow$ High

$\bar{x} \rightarrow 0$
 $x \rightarrow 1$

$$\bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}D + A\bar{B}C\bar{D}$$

I_1	I_2	I_3	I_4	O
A	B	C	D	Y

0	0	0	1	1
---	---	---	---	---

2	2	2	2
---	---	---	---

Position

0	1	0	1	1
---	---	---	---	---

$$2^0 = 1$$

$$100^0 = 1$$

0001
0101
0111
1000



What is POS?

→ POS (Product of Sum)

Diagram illustrating the formation of POS:

Sum terms (OR operation) are multiplied (AND operation) to form the Product of Sum (POS).

Example: $(A+B+C) \cdot (\bar{A}+B+C) \cdot (\bar{A}+\bar{B}+C)$

Where $(A+B+C)$ is M_1 , $(\bar{A}+B+C)$ is M_2 , and $(\bar{A}+\bar{B}+C)$ is M_3 .

As the name suggests, it is formed by multiplying (AND operation) the sum terms. These sum terms are also called as 'max-terms'. Maxterms are represented with 'M', they are the sum (OR operation) of Boolean variables either in normal form or complemented form.



Consider a function X, whose truth table is as follows:

A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

$\checkmark$ SOP
 A is High = A
 A is Low = $\bar{A}$

The function X can be written in POS form by multiplying all the max terms when X is LOW(0).

While writing POS, the following convention is to be followed:

A is Low = A
 A is High = $\bar{A}$

$$X(\text{POS}) = \prod_M(0, 2, 4, 5, 7)$$

$$= (A+B+C) \cdot (A+B'+C) \cdot (A'+B+C) \cdot (A'+B+C') \cdot (A'+B'+C')$$

$$X(\text{POS}) = \prod_m(0, 2, 4, 5, 7)$$

$\begin{matrix} 000 & 010 & 100 & 101 \\ \uparrow & \uparrow & \uparrow & \uparrow \\ 0 & 2 & 4 & 5 \end{matrix}$

POS $\rightarrow$ 0
 SOP $\rightarrow$ 1
 $(A+B+C) \cdot (\bar{A}+B\bar{C}) \cdot (\bar{A}\bar{B}\bar{C})$

$5 \rightarrow 101$
 $(\bar{A}+B\bar{C})$

SOP $\rightarrow$ represent Always High $\rightarrow$ 1 (output)

POS $\rightarrow$ represent Always Low $\rightarrow$ 0 (output)



Find the Expression :-

Q1:- $f(x,y,z) = \prod(0,4,6)$

000
100
110

$\Rightarrow (A+B+C) \cdot (\bar{A}+B+C) \cdot (\bar{A}+\bar{B}+C)$
 $\Rightarrow (x+y+z) \cdot (\bar{x}+y+z) \cdot (\bar{x}+\bar{y}+z)$

Q2:- $f(x,y,z) = \prod(1,5,7)$

001
101
111

$(x+y+\bar{z}) \cdot (\bar{x}+y+\bar{z}) \cdot (\bar{x}+\bar{y}+\bar{z})$

Q3:- $f(x,y,z) = \prod(1,5)$

001
101

$\Rightarrow (x+y+\bar{z}) \cdot (\bar{x}+y+\bar{z})$




S.No.	SOP	POS
1.	A way of representing Boolean expressions as sum of product terms.	A way of representing Boolean expressions as product of sum terms.
2.	SOP uses minterms. Minterm is product of Boolean variables either in normal form or complemented form.	POS uses maxterms. Maxterm is sum of Boolean variables either in normal form or complemented form.
3.	It is sum of minterms. Minterms are represented as 'm'	It is product of maxterms. Maxterms are represented as 'M'
4.	SOP is formed by considering all the minterms, whose output is HIGH(1)	POS is formed by considering all the maxterms, whose output is LOW(0)
5.	While writing minterms for SOP, input with value 1 is considered as the variable itself and input with value 0 is considered as complement of the input.	While writing maxterms for POS, input with value 1 is considered as the complement and input with value 0 is considered as the variable itself.



Minimization Of Boolean Expressions-

There are following two methods of minimizing or reducing the boolean expressions-

Methods To Minimize Boolean Expressions

 

1:-By using laws of Boolean Algebra

2:-By using Karnaugh Maps also called as K Maps



- 1:- K-Map is graphical representation used for simplifying the Boolean expressions
- 2:- For a Boolean Consisting of n -variables, number of cells required in K Map = 2^n cells.
- 3:-K-Map is based on Grey Code (Unit distance code).
- 4:- K-Map is based on three type of input values {0 , 1, don't care(x) }



Karnaugh Maps

- Another approach to simplification is called the Karnaugh map, or K-map.
- A K-map is a **truth table graph**, which aids in visually simplifying logic.
- It is useful for up to 5 or 6 variables, and is a good tool to help understand the process of logic simplification.
- The algebraic approach we have used previously is also used to analyze complex circuits in industry (computer analysis).
- At the right is a 2-variable K-map.
- This very simple K-map demonstrates that an n-variable K-map contains all the combination of the n variables in the K-map space.

	$\bar{y}$	y	
$\bar{x}$	00 0	01 1	This minterm is expressed as $f = \bar{x}y$
x	10 2	11 3	

Two-Variable K-map, labeled for SOP terms. Note the four squares represent all the combinations of the two K-map variables, or minterms, in x & y (example above).



Three-Variable Karnaugh Map

- A useful K-map is one of three variables.
- Each square represents a 3-variable minterm or maxterm.
- All of the 8 possible 3-variable terms are represented on the K-map.
- When moving horizontally or vertically, only 1 variable changes between adjacent squares, never 2. This property of the K-map, is unique and accounts for its unusual numbering system.
- The K-map shown is one labeled for SOP terms. It could also be used for a POS problem, but we would have to re-label the variables.

	yz	yz	yz	yz
x	000 0	001 1	011 3	010 2
x	100 4	101 5	111 7	110 6

As an example, this minterm cell (011) represents the minterm $f = xyz$.



Four Variable Karnaugh Map

- A 4-variable K-map can simplify problems of four Boolean variables.*
- The K-map has one square for each possible minterm (16 in this case).
- Migrating one square horizontally or vertically never results in more than one variable changing (square designations also shown in hex).

* Note that on all K-maps, the left and right edges are a common edge, while the top and bottom edges are also the same edge. Thus, the top and bottom rows are adjacent, as are the left and right columns.

	$\overline{y}z$	$\overline{y}z$	yz	yz
$\overline{w}x$	0000 0 0	0001 1 1	0011 3 3	0010 2 2
$\overline{w}x$	0100 4 4	0101 5 5	0111 7 7	0110 6 6
wx	1100 C 12	1101 D 13	1111 F 15	1110 E 14
wx	1000 8 8	1001 9 9	1011 B 11	1010 A 10

Note that this is still an SOP K-map.



Prime Implicants


- We will be simplifying Boolean functions plotting their values on a K-map and grouping them into prime implicants.
- What is a prime implicant? It is an implicant that covers as many 1 values (SOP K-map) or 0 values (POS K-map) as possible, yet still retains the identity of implicant (# of cells = power of 2, rectangular or square shape).
- Some SOP prime implicants are shown on the adjoining K-map.

	$\overline{y}z$	$\overline{y}z$	yz	yz
$\overline{w}x$	0000 1 0	0001 0 1	0011 1 3	0010 1 2
$\overline{w}x$	0100 1 4	0101 0 5	0111 1 7	0110 1 6
wx	1100 1 12	1101 1 13	1111 1 15	1110 1 14
wx	1000 1 8	1001 0 9	1011 0 11	1010 0 10



More Karnaugh Map Terminology

- Distinguished 1-cell: A single minterm that can be covered by only one prime implicant.
- Essential prime implicant: A prime implicant that covers one or more distinguished 1-cells.
- Note: Every fully minimized Boolean expression must include all of the essential prime implicants of f.
- In the K-map at right, the Boolean minterm $f = wxy\bar{z}$ is a distinguished 1-cell, and the essential prime implicant $f = wxy$ is the only prime implicant that includes it.

 



“Prime Implicants”

- As noted two slides back, a “prime implicant” is the largest square or rectangular implicant of cells occupied by a 1 (SOP) or 0 (POS). Thus a prime implicant will have 1, 2, 4, or 8 cells (16 is a trivial prime).
- How do we determine the Boolean expression for a prime implicant?
- The Boolean expression for an SOP prime implicant is determined by creating a new minterm whose only variables are those that do NOT change value (0→1 or 1→0) over the extent of the prime implicant.
- Thus the prime implicant at right may be represented by the Boolean expression: $f = xz$.

Since x & z do not change value over the implicant, they are the variables in the new Boolean minterm.

	$\overline{y}z$	$\overline{y}z$	$y\overline{z}$	$y\overline{z}$
$\overline{w}x$	0000 0 0	0001 1 1	0011 3 3	0010 2 2
$\overline{w}x$	0100 4 4	0101 5 1	0111 7 1	0110 6 6
wx	1100 C 12	1101 D 13	1111 F 15	1110 E 14
wx	1000 8 8	1001 9 9	1011 B 11	1010 A 10

Example of a prime implicant



Logic Simplification – an SOP Example

- We simplify a Boolean expression by finding its **prime implicants** on a K-Map.
- To do this, populate the K-map as follows:
 - For an SOP expression,* find the K-Map cell for each **minterm** of function f, and place a one (1) in it. Ignore 0's.
 - Circle groups of cells that contain 1's.
 - The number of cells enclosed in a circle must be a power of 2 and square or rectangular.
 - It is okay for groups of cells to overlap.
 - Each circled group of cells corresponds to a prime implicant of f.
 - Note that the more cells a given circle encloses, the fewer variables needed to specify the implicant!

	$\overline{y}z$	$\overline{y}z$	yz	yz
$\overline{W}X$	0000 0 0	0001 1 1	0011 3 3	0010 2 2
$\overline{W}X$	0100 4 1	0101 5 1	0111 7 1	0110 6 1
WX	1100 C 12	1101 D 13	1111 E 15	1110 E 14
WX	1000 8 8	1001 9 9	1011 B 11	1010 A 10

* A POS example will follow.



Using the K Map for Logic Simplification (2)

- Another example:
 - The implicants of f are 4, 6, 12, 14.
 - This corresponds to the function:

$$f = \overline{w}x\overline{y}z + \overline{w}xy\overline{z} + \overline{w}x\overline{y}z + \overline{w}xy\overline{z}$$
 - We create a prime implicant by grouping the 4 cells representing f .
 - On the wx axis, the cells are 1 whether or not w is one, and always when x is 1 (**w not needed**).
 - On the yz axis, the cells are 1 whether or not y is one, and always when z is 0 (**y not needed**).
 - Thus the simplified expression for f is: $f = x\overline{z}$.

	$\overline{y}z$	$\overline{y}z$	yz	yz
$\overline{w}x$	0000 0 0	0001 1 1	0011 3 3	0010 2 2
$\overline{w}x$	0100 4 1	0101 5 5	0111 7 7	0110 6 1
$\overline{w}x$	1100 C 1	1101 D 13	1111 F 15	1110 E 14
$\overline{w}x$	1000 8 8	1001 9 9	1011 B 11	1010 A 10

Remember: For purposes of grouping implicants, the top and bottom rows of the K-map are considered adjacent, as are the right and left columns. This grouping takes advantage of the fact that the left and right columns are adjacent.




A POS K-Map

- On a POS K-map, the procedure is the same, except that we map 0's.
- Let:

$$f = (\bar{w} + \bar{x} + \bar{y} + \bar{z}) \cdot (\bar{w} + \bar{x} + \bar{y} + z) \cdot (\bar{w} + \bar{x} + \bar{y} + z) \cdot (\bar{w} + \bar{x} + \bar{y} + z)$$
- We find prime implicants exactly the same way – except that we look for variable that produce 0's.
- As shown, w and y do not change over the extent of the function.
- The simplified expression is: $f = (\bar{w} + \bar{y})$. The simplified circuit is shown at right.

	$y + z$	$y + \bar{z}$	$\bar{y} + \bar{z}$	$\bar{y} + z$
$w + x$	0000 0 0	0001 1 1	0011 3 3	0010 2 2
$w + \bar{x}$	0100 4 4	0101 5 5	0111 7 7	0110 6 6
$\bar{w} + \bar{x}$	1100 C 12	1101 D 13	1111 F 15	1110 E 14
$\bar{w} + x$	1000 8 8	1001 9 9	1011 B 11	1010 A 10

 



Summary of Karnaugh Map Procedure

- In summary, to simplify a Boolean expression using a K-Map:
 1. Start with the truth table or Boolean expression, if you have one.
 2. If starting from the truth table, write the Boolean expression for each truth table term that is 1 (if SOP) or 0 (if POS).
 3. (Develop the full Boolean expression, if necessary, by OR-ing the AND terms together if SOP or AND-ing OR terms if POS.)
 4. On the K-Map, plot 1's (for SOP) or 0's (for POS).
 5. Group implicants together to get the largest set of prime implicants possible. Prime implicants may overlap each other. They will always be square or rectangular groups of cells that are powers of 2 (1, 2, 4, 8).
 6. The variables that make up the term(s) of the new expression will be those which do not vary in value over the extent of each prime implicant.
 7. Write the Boolean expression for each prime implicant and then OR (for SOP) or AND (for POS) terms together to get the new expression.



K-Map Example of Prime Implicants

- The Boolean expression represented is:

$$f = \overline{w}x\overline{y}z + \overline{w}xy\overline{z} + \overline{w}xy\overline{z} + \overline{w}x\overline{y}z + wxy\overline{z} + wxy\overline{z} + wx\overline{y}z + wx\overline{y}z$$
- Note that since prime implicants must be powers of 2, the largest group of squares we can circle is 4.
- Thus we circle three groups of 4 (in red). The circles may overlap.
- We now write the new SOP simplified expression. It is:

$$f = xy + xz + wz$$

	$\overline{y}z$	$\overline{y}z$	yz	yz
$\overline{w}x$	0000 0 0	0001 1 1	0011 3 3	0010 2 2
$\overline{w}x$	0100 4 4	0101 5 1	0111 7 1	0110 6 1
$\overline{w}x$	1100 C 12	1101 D 13	1111 F 15	1110 E 14
$\overline{w}x$	1000 8 8	1001 9 1	1011 B 11	1010 A 10

NOT a prime implicant!



Another SOP Minimization, Given the Truth Table

w	x	y	z	f
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	1
0	1	0	1	1
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	1
1	1	0	1	1
1	1	1	0	
1	1	1	1	

Minterms Plotted on K-Map

- The four minterms are plotted on the truth table.
- Note that they easily group into one prime implicant.
- Over the extent of the prime implicant, variables w & z vary, so they cannot be in the Boolean expression for the prime implicant.
- Variables x and y do not vary.
- Thus the expression for the minimum SOP representation must be $f = \overline{x}y$.

	$\overline{y}z$	$\overline{y}z$	$y\overline{z}$	yz
$\overline{w}x$	0000 0 0	0001 1 1	0011 3 3	0010 2 2
$\overline{w}x$	0100 1 4	0101 5 5	0111 7 7	0110 6 6
wx	1100 12 12	1101 13 13	1111 15 15	1110 14 14
wx	1000 8 8	1001 9 9	1011 11 11	1010 10 10

The original Boolean expression is:
 $f = \overline{w}x\overline{y}z + \overline{w}xy\overline{z} + wx\overline{y}z + wx\overline{y}\overline{z}$



Another Example: Biggest Prime Implicants

w	x	y	z	f
0	0	0	0	
0	0	0	1	1
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	1
0	1	1	0	
0	1	1	1	1
1	0	0	0	
1	0	0	1	1
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	1
1	1	1	0	
1	1	1	1	1

Minimization Using Four-Variable K-Map

	$\overline{yz}$	$\overline{yz}$	yz	yz
$\overline{WX}$	0000 0 0 1 1	0001 1 3 3 2 2	0011	0010
$\overline{WX}$	0100 4 4 5 5 7 7 6 6	0101 1 5 5 7 7 6 6	0111 1 7 7 6 6	0110
$\overline{WX}$	1100 C 12 D 13 E 14	1101 1 D 13 E 14	1111 1 E 14	1110
$\overline{WX}$	1000 8 8 9 9 B 11 A 10	1001 1 9 9 B 11 A 10	1011	1010

Incorrect solution (partial minimization): $f = xyz + yz$

	$\overline{yz}$	$\overline{yz}$	yz	yz
$\overline{WX}$	0000 0 0 1 1	0001 1 3 3 2 2	0011	0010
$\overline{WX}$	0100 4 4 5 5 7 7 6 6	0101 1 5 5 7 7 6 6	0111 1 7 7 6 6	0110
$\overline{WX}$	1100 C 12 D 13 E 14	1101 1 D 13 E 14	1111 1 E 14	1110
$\overline{WX}$	1000 8 8 9 9 B 11 A 10	1001 1 9 9 B 11 A 10	1011	1010

Correct Solution:
 $f = xz + \overline{yz}$

Remember: Prime implicants should overlap, if this means that they can be made larger.



The Concept of “Don’t Cares”

- The six implicants on the K-Map shown can be represented by the simplified expression $f = x y + x z$.
- Suppose for our particular logic system, we know that y and z will never be 0 together.
- Then the yz implicants do not matter, since they cannot happen.
- To show the condition cannot occur, we put X 's in the column -- they are “don't cares” -- conditions that cannot happen.

	$\overline{y}z$	$\overline{y}z$	yz	$y\overline{z}$
$\overline{w}x$	0000 0 X 0	0001 1 1	0011 3 3	0010 2 2
$\overline{w}x$	0100 4 X 4	0101 5 5	0111 7 7	0110 6 6
wx	1100 C X 12	1101 D 13	1111 F 15	1110 E 14
wx	1000 8 X 8	1001 9 9	1011 B 11	1010 A 10



“Don’t Cares” (2)

- Since the function will never get into the left column, we “don’t care” how those minterms are represented.

Why not make them 1's?

- Doing that, we can make a much larger prime implicant and a simpler Boolean expression. **For this implicant, $f = X$.**

- The expression is valid, since the forbidden condition will never allow the two left squares to be occupied.
- “Don’t cares” let us further simplify an expression.

	$\overline{y}z$	$\overline{y}z$	yz	$y\overline{z}$
$\overline{W}X$	0000 0 1 0	0001 1 1 1	0011 3 3 3	0010 2 2 2
$\overline{W}X$	0100 4 1 4	0101 5 1 5	0111 7 1 7	0110 6 1 6
WX	1100 C 1 12	1101 D 1 12	1111 F 1 12	1110 E 1 11
WX	1000 8 1 8	1001 9 9 9	1011 B 11 11	1010 A 10 10



“Don’t Cares” – Another Example

- Assume the Boolean expression is as shown on the K-map (black 1's and black prime implicants).
- The simplest SOP expressions for the function is $f = wxz + wxy$.
- Also assume that $wx\bar{y}z$ and $wx\bar{y}\bar{z}$ cannot occur.
- Since these cannot ever happen, they are “don’t cares,” and since they are “don’t cares,” make them 1 (**red**)!
- We can then further simplify the expression to $f = wx + xz$ (larger prime implicants).

	$\bar{y}z$	$\bar{y}\bar{z}$	yz	$y\bar{z}$
$\bar{w}x$	0000 0 0	0001 1 1	0011 3 3	0010 2 2
$\bar{w}x$	0100 4 4	0101 5 5	0111 7 7	0110 6 6
wx	1100 C 12	1101 D 13	1111 F 14	1110 E 11
wx	1000 8 8	1001 9 9	1011 B 11	1010 A 10



“Don’t Cares” -- Summary

- “Don’t Cares” occur when there are variable combinations, represented by squares on a Karnaugh map, that cannot occur in a digital circuit or Boolean expression.
- Such a square is called a “Don’t Care.” Since it can never happen, we can assign a value of 1 to the square and use that 1 to (possibly) construct larger prime implicants, further simplifying the circuit (you could assign it the value 0 in a POS representation).
- Circuits or Boolean expressions derived using “Don’t Care” squares are as valid as any other expression or circuit.
- We will see later in sequential logic that the concept of “Don’t Cares” will help in simplifying counter circuits.

THANK YOU